

CENG 311

Computer Architecture Lab

Logic Design Review

2023-2024

Fall

Digital Electronics

- Digital electronics operate on 2 voltage levels: high and low.
- Binary systems: 1 or 0 , true or false, asserted or deasserted
- Values 0 and 1 are called as **complement** or **inverses** of one another.

Number Conversions

- **Decimal** -> Base 10; 1,56,798,...
- **Binary** -> Base 2; 0000, 001001,...
- **Octal** -> Base 8; 01,02,...
- **Hexadecimal (Hex)** -> Base 16; 0A, ABCD, FFFF,...

Binary- Hex Conversion

Hex	Decimal	Binary
0	0	0000
1	1	0001
2	2	0010
3	3	0011
4	4	0100
5	5	0101
6	6	0110
7	7	0111
8	8	1000
9	9	1001
A	10	1010
B	11	1011
C	12	1100
D	13	1101
E	14	1110
F	15	1111

Example:

$$(0001001010111111)_2 = \underbrace{0001}_1 \underbrace{0010}_2 \underbrace{1011}_B \underbrace{1111}_F$$

$$(0001001010111111)_2 = (12BF)_{16}$$

Logic Functions and Gates

- **AND Operator:** $A * B$, logical product

AND Gate:



AND Truth Table

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

- **OR Operator:** $A + B$, logical sum

OR Gate:



OR Truth Table

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

NOT operator: \bar{A}


NOT Gate:




NOT Truth Table

A	B
0	1
1	0


Multiplexer (Mux)

 

1-bit 2x1 Mux

 


32-bits 2x1 Mux

 

4-bits 2x1 Mux

Basic Arithmetic and Logic Unit (ALU)

 

1 bit ALU

Binary Addition- Half Adder



Inputs		Outputs	
A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Binary Addition- Full Adder

Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	$0 + 0 + 0 = 00_{\text{two}}$
0	0	1	0	1	$0 + 0 + 1 = 01_{\text{two}}$
0	1	0	0	1	$0 + 1 + 0 = 01_{\text{two}}$
0	1	1	1	0	$0 + 1 + 1 = 10_{\text{two}}$
1	0	0	0	1	$1 + 0 + 0 = 01_{\text{two}}$
1	0	1	1	0	$1 + 0 + 1 = 10_{\text{two}}$
1	1	0	1	0	$1 + 1 + 0 = 10_{\text{two}}$
1	1	1	1	1	$1 + 1 + 1 = 11_{\text{two}}$



Binary Addition- Full Adder

A	B	C _{in}	SUM (S)	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 
 


$$C_{out} = \bar{A}.B.C_{in} + A.\bar{B}.C_{in} + A.B.\bar{C}_{in} + A.B.C_{in} \quad S = \bar{A}.\bar{B}.C_{in} + \bar{A}.B.\bar{C}_{in} + A.\bar{B}.\bar{C}_{in} + A.B.C_{in}$$

Binary Addition- Full Adder

  

1-bit ALU Unit with Adder Circuit

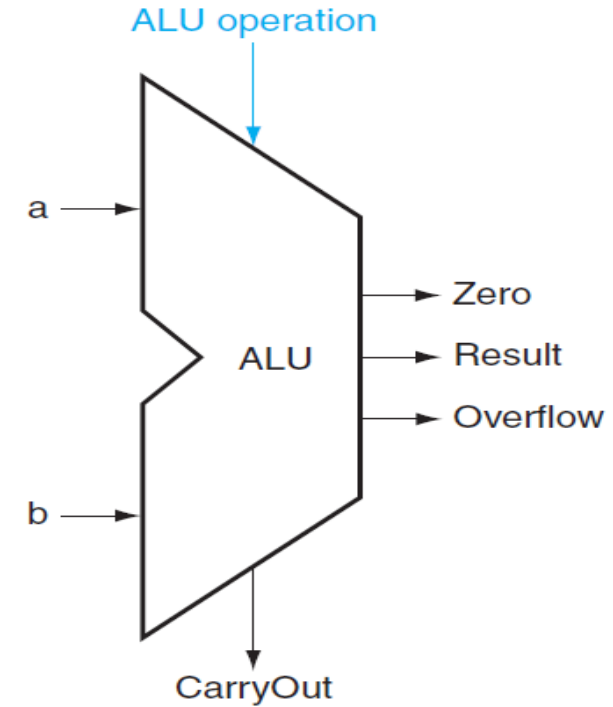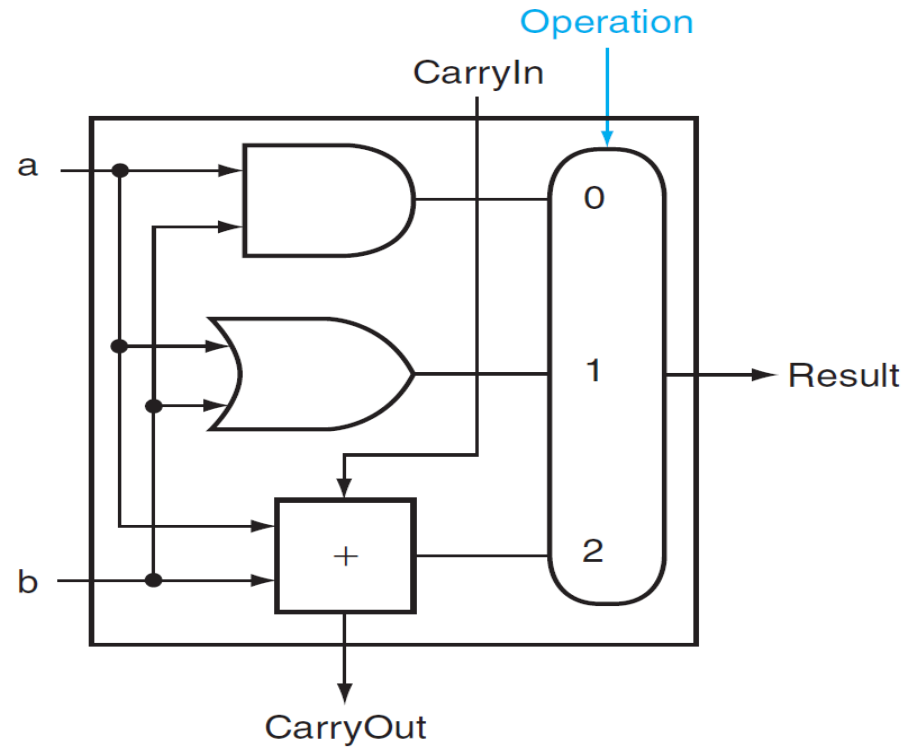

Binary Subtraction


- Use 2's complement format:
 1. Invert each bits (take the 1's complement)
 2. Add 1.

Example: Write -5 in binary format.

$$(5)_{10} = 0101$$


1. Take 1's complement: 1010
2. Add 1 : $(1011)_2 = (-5)_{10}$

ALU with binary subtraction

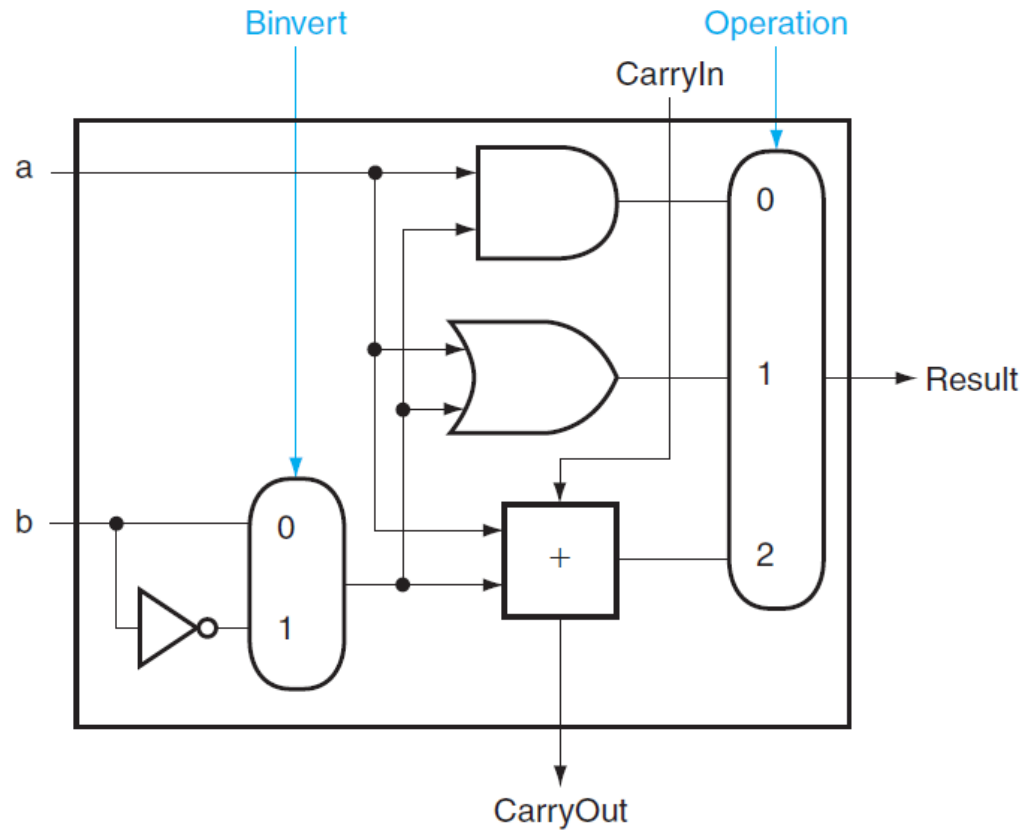

Clocks

 - Clocks are used in sequential logic in order to decide when an element that contains **state** should be updated.
- **Edge triggered clocking:** state changes occurs on clock edges.




$$\text{Clock Frequency} = 1 / \text{clock period}$$

Flip-Flops – D Flip-Flop


- A kind of memory component that can hold 1 bit data
- D flip flops used in;
 - ☐ Memory
 - ☐ Registers
 - ☐ Counters

Flip-Flops – D Flip-Flop


D	CLK	Q	Q'
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

 


Register File

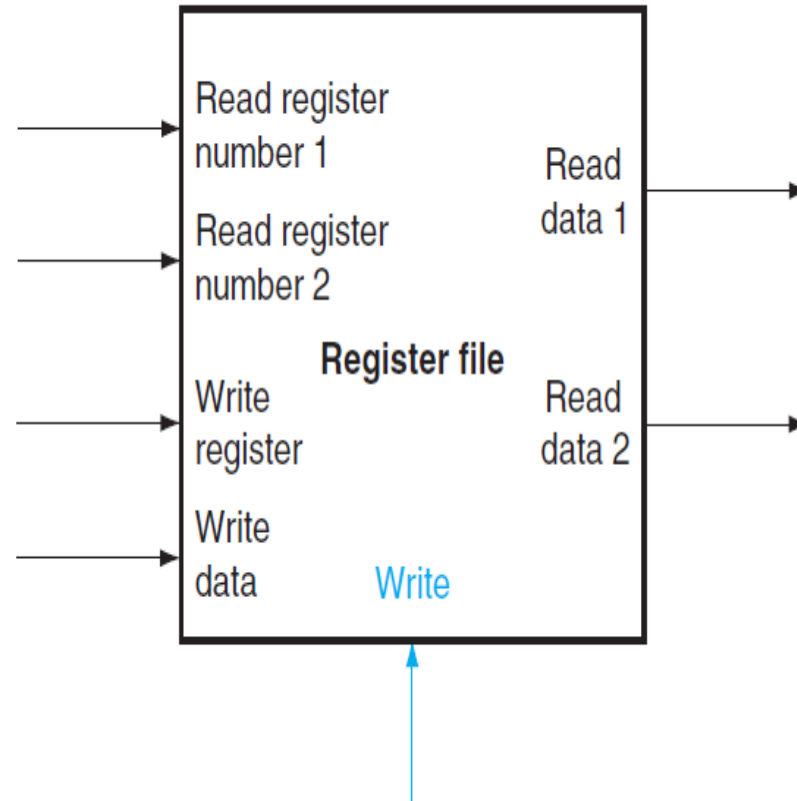

Read Register

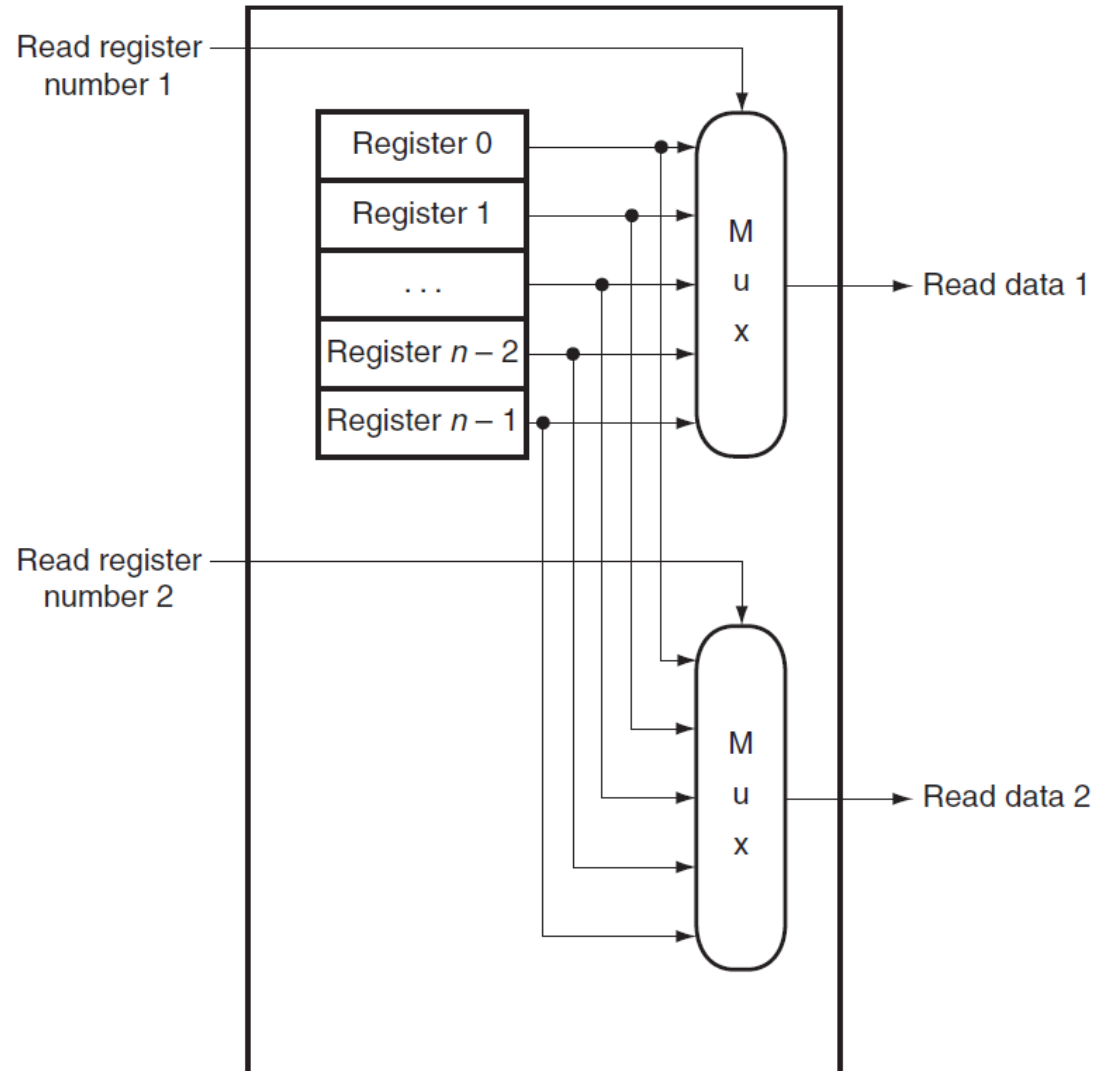


Write Register

 


a. A 3-bit decoder

Inputs			Outputs							
12	11	10	Out7	Out6	Out5	Out4	Out3	Out2	Out1	Out0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

b. The truth table for a 3-bit decoder

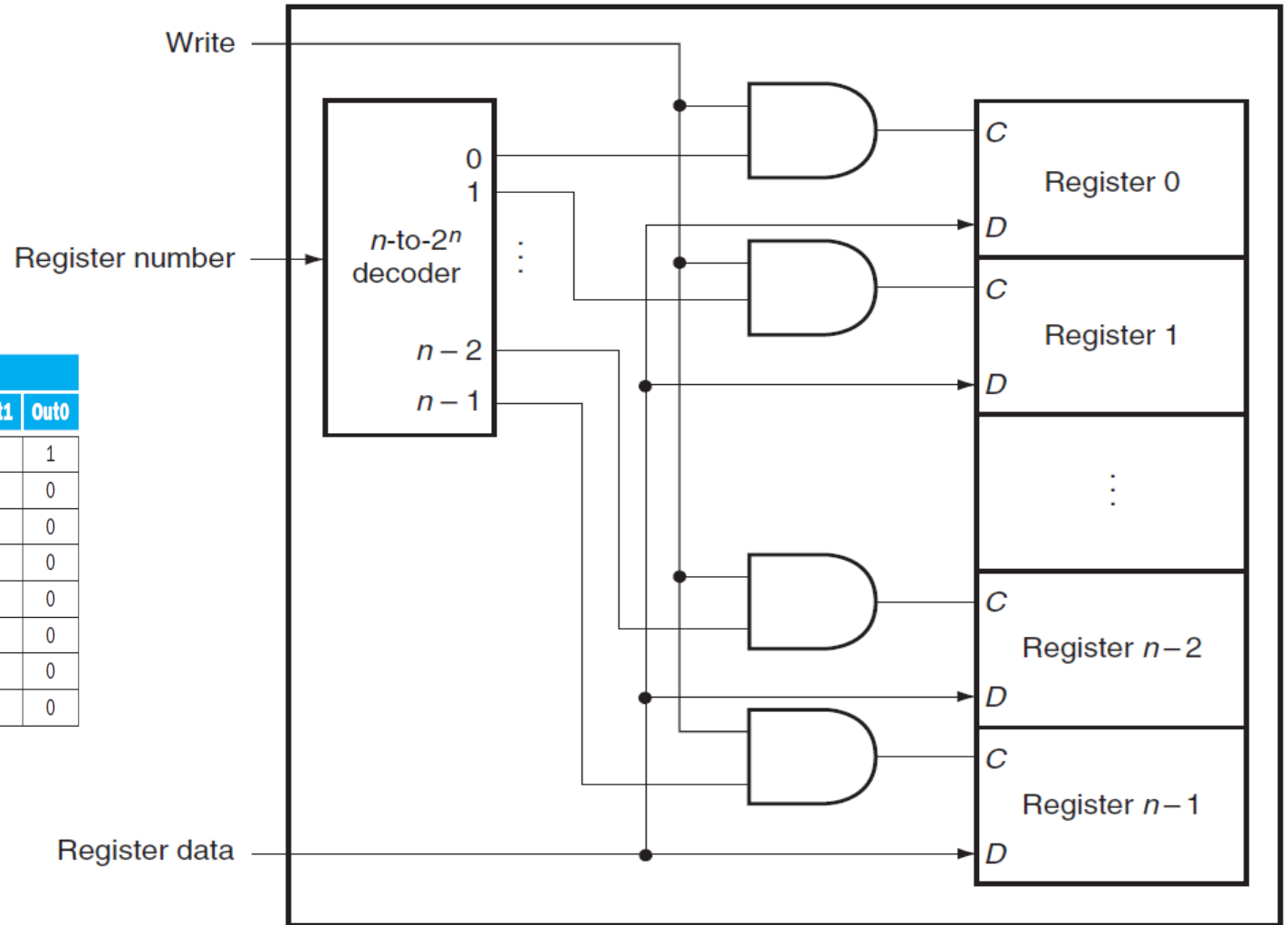


Memory address

 


1 Word = 4 bytes = 32 bits
1 byte = 8 bits

Little Endian- Big Endian

Data = 01234567

 

Big Endian

 

Little Endian