

CENG 311


Computer Architecture

LAB 9

Instruction Addition to MIPS Single Cycle Datapath

Jump-Jal-Jr

Implementing Jumps

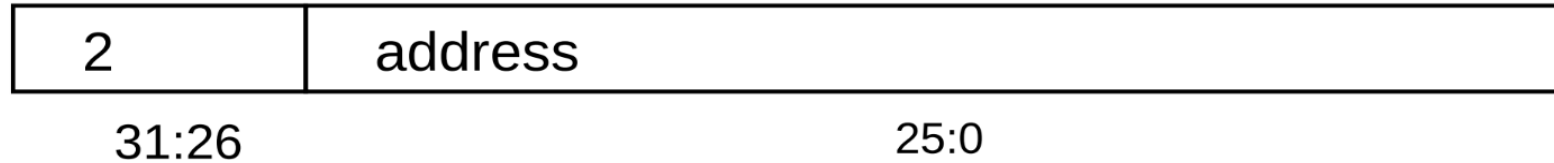

Jump uses word address

Update PC with concatenation of


Top 4 bits of old PC

26-bit jump address

The bits 00 (shift left 2)

Need an extra control signal decoded from opcode


Datapath with Jumps

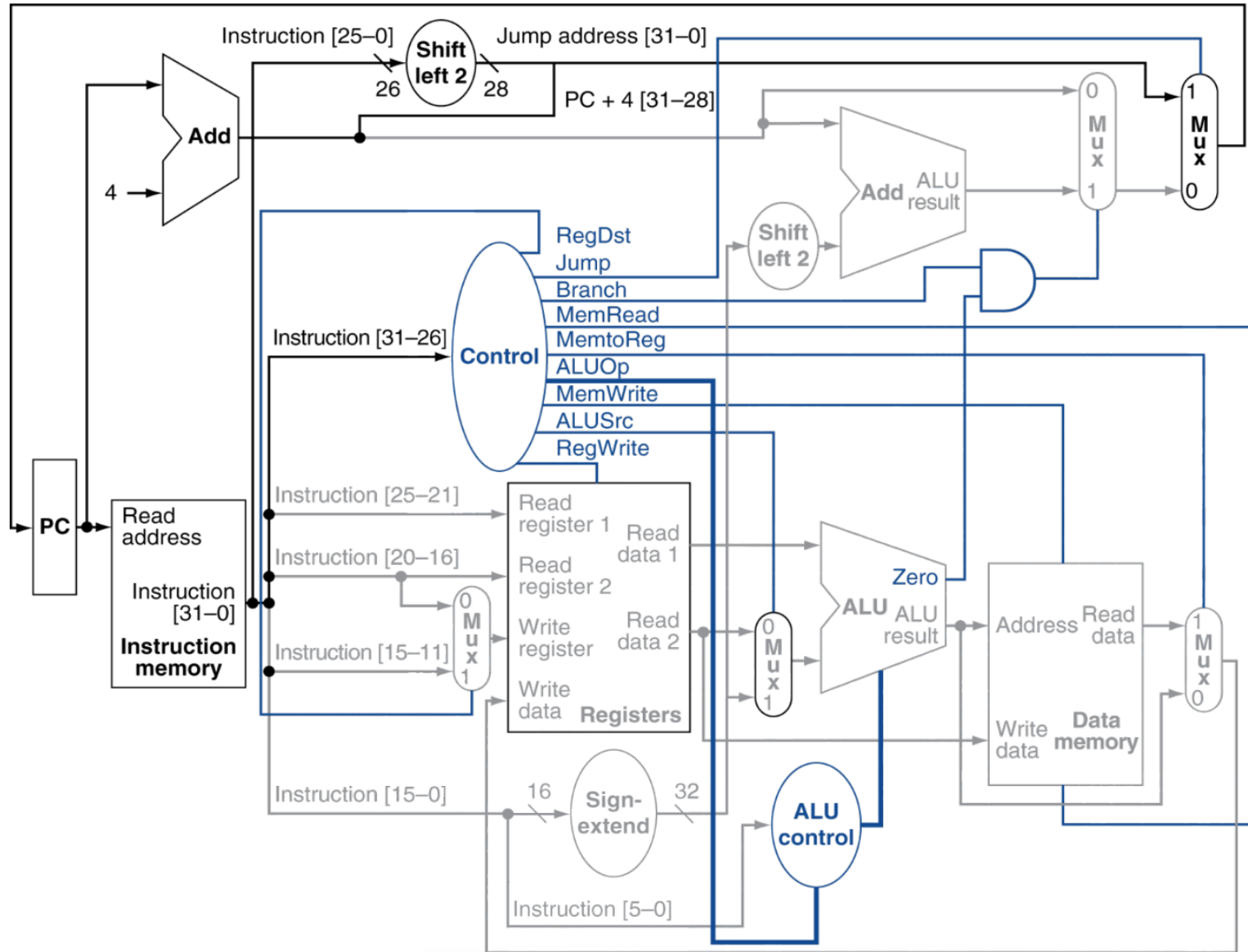

Implementing jal (jump and link)

- Saves the return address (**PC+4**) to \$ra register before jumping to the target address.

Jump and link

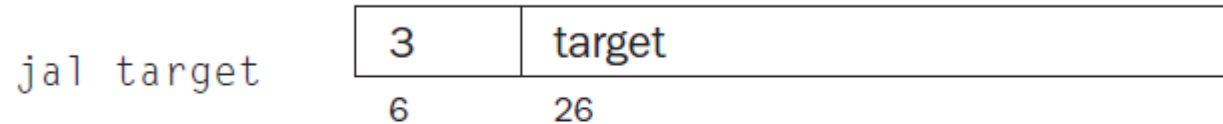

Unconditionally jump to the instruction at target. Save the address of the next instruction in register \$ra.

Implementing jr (jump register)

Jump register

jr rs

0	rs	0	8
6	5	15	6

Unconditionally jump to the instruction whose address is in register rs.

jr \$ra (register 31)

op	rs	rt	rd	shamt	funct
0	31	0	0	0	8
000000	11111	00000	00000	00000	001000